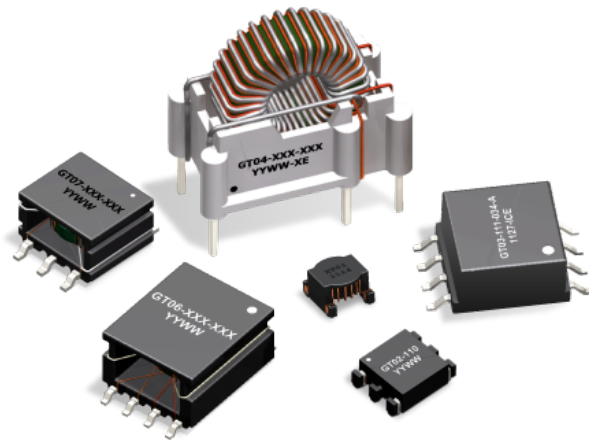


Applying Gate Drive Transformers in Push-Pull Topology as the High-Side and Low-Side Drivers

Application Information



1 Introduction

Gate Drive Transformers (GDTs) provide galvanic isolation, level shifting and common-mode noise immunity between low-voltage control electronics and power semiconductors (MOSFETs, IGBTs, SiC devices). In push-pull gate-drive topologies, a GDT replicates the drive waveform from the primary to one or more isolated secondaries, supporting both high-side (floating) and low-side (ground-referenced) gates.

Careful selection of transformer parameters – including turns ratio, volt-time (ET) rating, leakage inductance, interwinding capacitance, creepage and clearance distances, and insulation system – play a critical role in ensuring reliable switching performance, minimizing dynamic losses, and maintaining electromagnetic compatibility (EMC). ICE Components offers a versatile lineup of surface-mount (SMT) and through-hole (THT) gate drive transformers ([GT02](#), [GT03](#), [GT04](#), [GT06](#), [GT07](#), [GT17005](#), etc.) engineered for reinforced isolation, low leakage inductance, and automotive-grade durability.

2 Push-Pull Topology Overview

Operating Principle:

- A push-pull power topology operates by alternately switching two transistors (or switches) that drive current in opposite directions through a center-tapped transformer, efficiently transferring energy to the load while utilizing both halves of the transformer core.
- The GDT replicates the control IC signal from the primary to the secondary winding(s) while maintaining isolation.
- High-side drive delivers the gate signal to a floating reference; low-side drive delivers it to a ground-referenced device.

Key Advantages:

- Eliminates complex high-side driver ICs with bootstrap circuits.
- Provides excellent common-mode noise rejection.
- Enables high-speed signal transfer with low propagation delay.
- Can meet reinforced isolation requirements with appropriately rated windings and creepage.

3 High-Side vs Low-Side Drive Requirements

$$ET = \frac{E_p}{2f} \quad \text{or} \quad ET = E_p \cdot T_{ON}$$

Where: E_p = Drive voltage; T_{ON} = On-time per cycle;
 f = Operating frequency.

Similarities:

- Low leakage inductance is essential for fast gate transitions, reduced switching losses, and EMI control.
- Configurable turns ratios (e.g., 1:1, 1:1.5) support direct or level-shifted gate voltages for MOSFETs, IGBTs, and SiC devices.
- ET rating must meet gate timing demands
- Hi-Pot rating should exceed regulatory requirements.
- Maintain layout spacing to preserve isolation and minimize capacitive coupling.

Turns Ratio:

Defines the relationship between primary and secondary voltages.

$$E_s = \frac{E_p \cdot N_s}{N_p}$$

Where: E_s = Gate voltage; E_p = Drive voltage;
 N_s = Secondary Turns; N_p = Primary Turns.

High-Side Drive:

- May require extended creepage and clearance to meet reinforced isolation standards. The exact requirements depend on your safety system classification.

Practical Guidelines:


- 1:1 is common for MOSFET gates (e.g., primary drive $\pm 10\text{--}15\text{ V}$ \rightarrow secondary $\pm 10\text{--}15\text{ V}$).
- Ratios $>1:1$ step the V_G up (e.g., 1:1.5 to raise a 15 V primary to $\approx 22.5\text{ V}$ secondary) when needed for particular devices.

Low-Side Drive:

- Creepage and clearance may be less stringent. However, if both transformers share a common driver IC and safety isolation boundary (e.g., between control electronics and the power stage), then both may need similar creepage.

Creepage and Clearance:

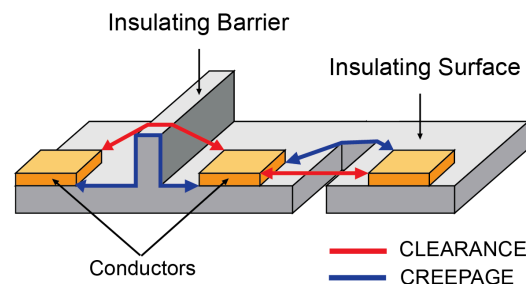Creepage is the shortest path along an insulating surface between conductors, while clearance is the shortest distance through air between them.



4 Design Considerations

Voltage-Time (ET) Product:

Avoid core saturation by selecting a GDT with a volt-second (ET) rating greater than the applied primary volt-seconds.

Typical guideline ranges (system dependent):

- **Si MOSFETs:** ~3–6 mm creepage
- **IGBTs:** ~6–8 mm creepage
- **SiC MOSFETs:** ~8–12 mm creepage

Example: ICE’s GT06 family with 12.5 mm creepage supports reinforced isolation in demanding environments.

5 GDT Suitability

Selecting an appropriate GDT requires consideration of the target switching device. The following guidelines outline GDT suitability across different device types.

- **Si MOSFETs:** $V_G \approx +10\text{--}12\text{ V}$; low gate charge (Q_G); high switching frequency – very suitable for GDTs.
- **IGBTs:** $V_G \approx +15\text{ V}$ (on), $-5\text{ to }-15\text{ V}$ (off); high gate charge; lower switching speed – possible with large ET and energy handling.
- **SiC MOSFETs:** $V_G \approx +18\text{--}20\text{ V}$ (on), $-3\text{ to }-5\text{ V}$ (off); moderate gate charge; very fast switching – feasible but demanding; leakage, overshoot and ET margin critical; isolated IC drivers are often preferred.

6 Example Application

Specifications:

- Input: 400 V_{DC}
- Output: $\pm 15\text{ V}_{DC}$
- Gate Drive Voltage: 12V
- Power Rating: 200 W
- Switching Frequency: 200 kHz
- Switches: N-channel (Si) MOSFETs

Implementation:

For a push-pull topology, each switch conducts for half the switching period.

$$t_{ON} = \frac{1}{2f} = \frac{1}{2(200,000)} = 2.5\mu\text{s}$$

So the required ET to fully enhance the MOSFET gate is $ET = 12\text{ V} \times 2.5\mu\text{s} = 30.0\text{ V}\cdot\mu\text{s}$.

Part Recommendations:

- **Gate Drive Transformer – GT06 Series** (High-Side and Low-Side)

This GDT family is suitable for both high-side and low-side drive in systems requiring reinforced isolation and high dv/dt immunity. Select a variant with:

- Turns ratio: 1:1 for direct $\pm 12\text{ V}$ gate coupling
- $ET \geq 49\text{ V}\cdot\mu\text{s}$ (includes margin for tolerances and transients)
- Creepage $\geq 12.5\text{ mm}$
- Hi-pot rating: 3750 VAC
- **Action Items and Selection Checklist**
 - Confirm primary driver amplitude E_p and compute required secondary E_s using $E_s = E_p \times (N_s/N_p)$.
 - Verify $ET \geq E_p \times t_{ON}$ (example: $12\text{ V} \times 2.5\mu\text{s} = 30.0\text{ V}\cdot\mu\text{s}$) including margin for tolerances and transients.
 - Check leakage inductance, tested gate transition with chosen switching device and gate resistor, and EMI impact.
 - Confirm creepage, clearance, and hi-pot meet system isolation requirements (example: using GT06 for reinforced isolation).
 - If a standard part does not meet turns ratio or ET needs, you may **request a custom GDT** from ICE Components.

7 Conclusion

Selecting GDTs with the appropriate ET rating, turns ratio, leakage inductance, and creepage distance ensures reliable, efficient operation across a range of switching devices — including Si MOSFETs, IGBTs, and SiC MOSFETs. While GaN HEMTs typically require IC-based isolated drivers due to their low voltage tolerance and ultra-fast switching, transformer-based solutions remain highly effective for most silicon and wide-bandgap applications.

ICE Components' GT06 (reinforced isolation, higher ET, larger creepage) and GT02 (compact, low-profile) families are proven starting points for push-pull gate-drive implementations; please verify ET and turns ratio for your exact gate energy and switching frequency and **contact ICE Components** for custom windings if needed.

For more details about our GDTs, please visit:

<https://www.icecomponents.com/product-category/transformers/gate-drive-transformers/>

Disclaimer

The information contained in this document is provided for general reference and design guidance only. While ICE Components strives to ensure the accuracy and reliability of the information presented, no guarantees or warranties, express or implied, are made regarding its completeness, accuracy, or suitability for any particular application.

Designers are responsible for independently evaluating, validating, and testing all products and circuits used in their applications to ensure compliance with applicable performance, safety, regulatory, and environmental requirements.

Product specifications, availability, and performance characteristics are subject to change without notice. ICE Components assumes no liability for any damages, losses, or claims arising from the use of the information contained in this document or the use of any products referenced herein.

For the latest product information, datasheets, and application support, please visit www.icecomponents.com or [contact ICE Components](#) directly.